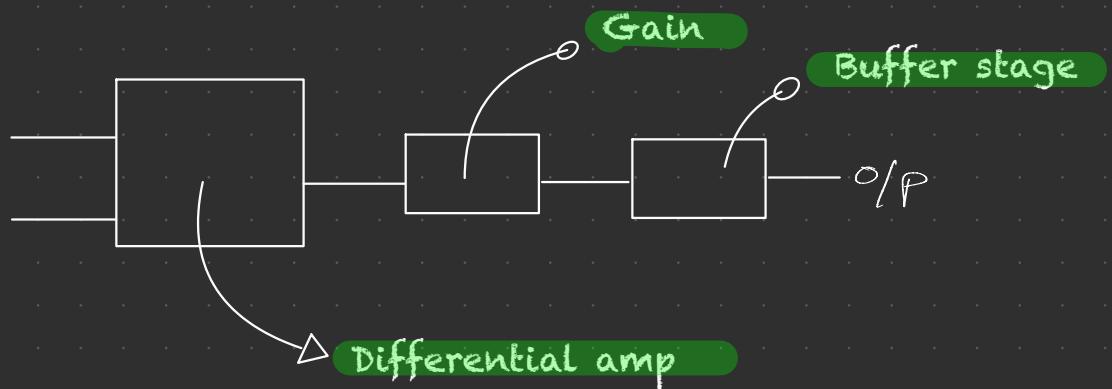




Design of two stage op-amp

Op-amp design



Specification

UMC 180 nm process

V_{DD} = 1.8V

A_v = 100 40 dB

C_L = 10 pF

I_{CMR} = ± 1.6V


I_{CMR} = 0.8V

S_R = 5V/usec

Power < 3 mW

Gain b.w = 5GHz

Differential amplifier part

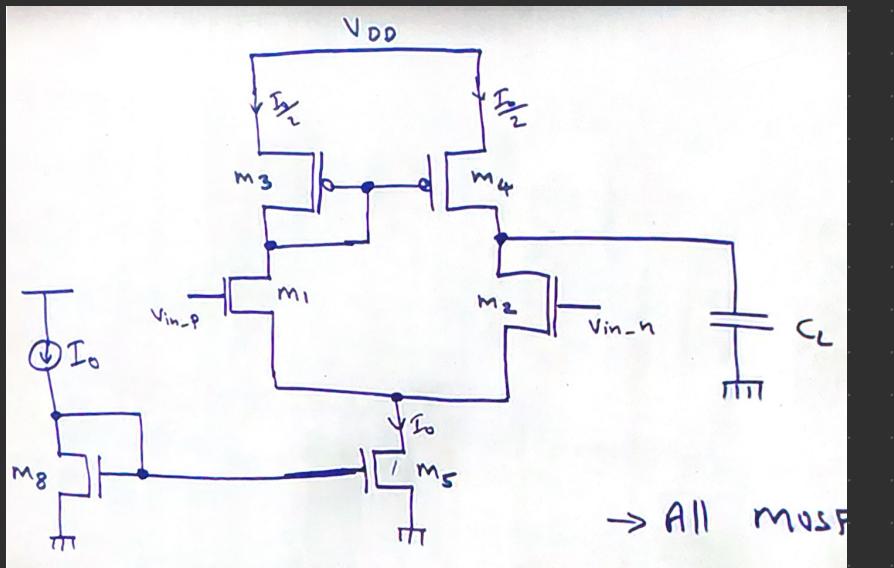

$$\left. \begin{array}{l} m_3 = m_4 \\ m_1 = m_2 \end{array} \right\}$$

We need to find W/L

① Steps to follow:

UMC 180 nm process

VDD = 1.8V

AV = 100 40 dB

CL = 10 pF

ICMR + = 1.6V

ICMR - = 0.8V

SR = 5V/usec

Power < 3 mW

Gain b.w = 5 MHz

① All MOSFET should be in "Saturation

Region"

② I_o → Slew Rate


③ M_3, M_4 → ICMR + (max)

④ M_1, M_2 → Gain × B.W

⑤ M_8 → I_o & M_5

① Finding I_o From Slew Rate %

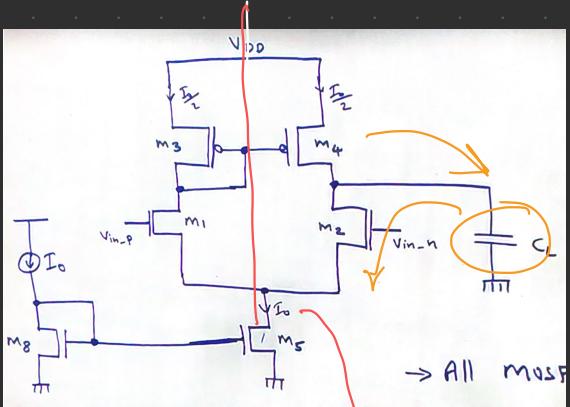Slew rate max change of o/p voltage
 UMC 180 nm process
 $V_{DD} = 1.8V$
 $A_v = 100 \text{ dB}$
 $C_L = 10 \text{ pF}$
 $ICMR = 1.6V$
 $ICMR = 0.8V$
 $SR = 5V/\mu\text{sec}$
 Power < 3 mW
 Gain bw = 5 MHz



→ charging of C_L is through M_1 ,
 discharging through M_2

$$Q = CV$$

$$\frac{dQ}{dt} = I = C \cdot \frac{dV}{dt}$$

$$I_o = 5 \times 10^6 \times 10 \times 10^{-12}$$


$$= 50 \times 10^{-6}$$

$$I_o = 50 \mu\text{A}$$

$$\frac{dV}{dt} = \frac{I}{C} = \frac{50 \mu\text{A}}{10 \text{ pF}}$$

$$\text{Slew rate} = \frac{I}{C}$$


$$I_o = SR \times C_L$$

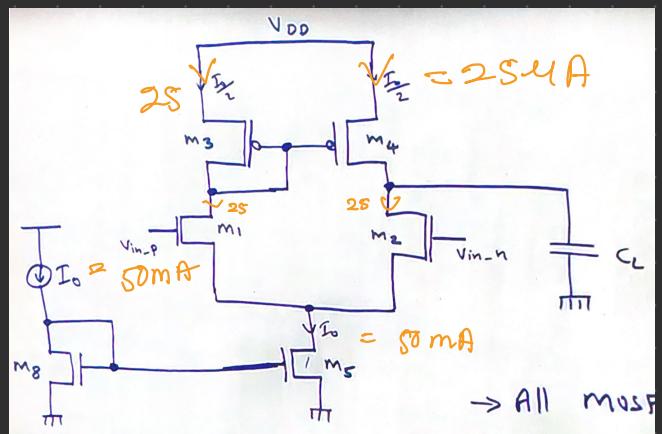

② M_3, M_4 From ICMR (+ve)

$$M_3 = M_4$$

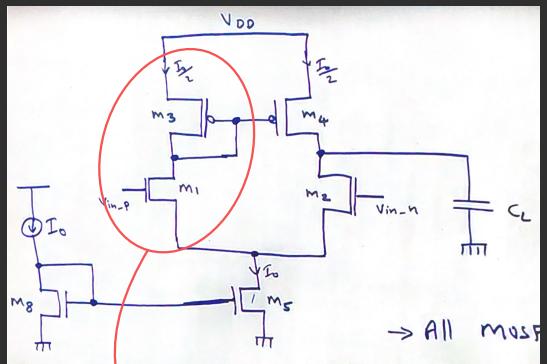UMC 180 nm process
 $V_{DD} = 1.8V$
 $A_v = 100 \text{ dB}$
 $C_L = 10 \text{ pF}$
 $ICMR_{+} = 1.6V$
 $ICMR_{-} = 0.8V$
 $SR = 5V/\mu\text{sec}$
Power < 3 mW
Gain bandwidth = 5 MHz




③ What should be the maximum value of V_{in} , to keep M_3 in "saturation".

$$V_D \geq V_g - V_t$$

$$V_X \geq \text{ICMR (+ve)} - V_t \quad (\text{max})$$

$\downarrow V_{in}$

$$V_X \geq 1.6 - 0.45 \approx 1.15V$$

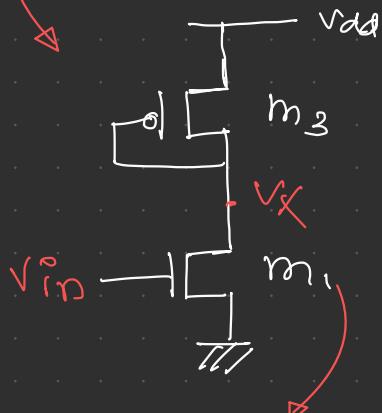

$$V_{DS} \geq V_{GS} - V_t$$

$$V_X \simeq 1.2 > 1.15$$

$$V_{DS} \Big|_{M3} = V_{dd} - V_x \begin{cases} \text{diode} \\ \text{connected} \end{cases}$$

$$= 1.8 - 1.2 = 0.6$$


~~APP~~

$$V_{DS} = 0.6V$$

$$I_D = \frac{S_0}{2} = 25 \mu A$$

M_3, M_4

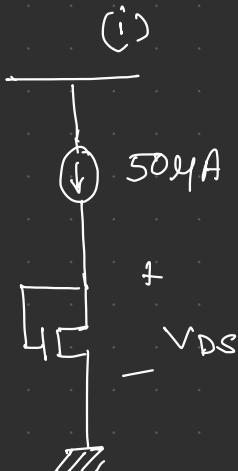① Finding $\mu_n C_{ox}$ & $\mu_p C_{ox}$ Using Cadence




$$\beta_{eff} = \mu_p C_{ox} \left(\frac{W}{L}\right)_{eff} \simeq 600 \text{ mA} \\ \text{---> } L_0 \simeq \text{copper thickness}$$

$$\mu_p C_{ox} = 600 \text{ mA} \quad \boxed{\mu_n C_{ox} = 300 \text{ mA/V}}$$

$$V_{tp} = 0.5 \text{ V}$$

$$V_{tn} = 0.4 \text{ V}$$

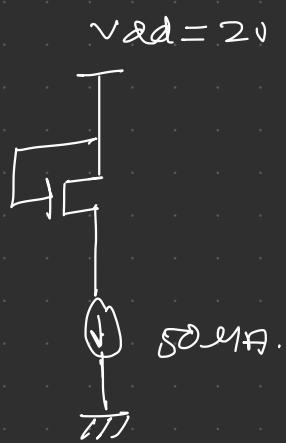


$$\text{Find } \left(\frac{W}{L}\right)_{m_3} = I_3 = \frac{\mu_p C_{ox} \left(\frac{W}{L}\right)}{2} [V_{GS} - V_t]^2$$

$$\text{or } 25 \text{ mA} = \frac{600 \text{ mA}}{2} \left[\frac{0.6 - 0.5}{\text{---> PMOS}}\right]$$

$$\left(\frac{W}{L}\right) = 83.33 \simeq 84$$


$$\boxed{\left(\frac{W}{L}\right)_{m_3, m_4} = 84}$$

m_3, m_4 are
symmetrical also
p-MOS

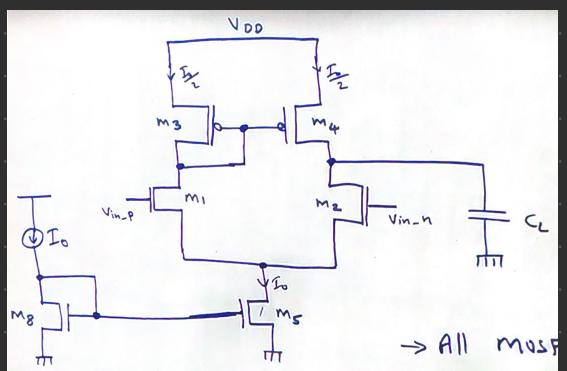

⑥ Find m_1 , m_2 :

From Gain Bandwidth parameter.

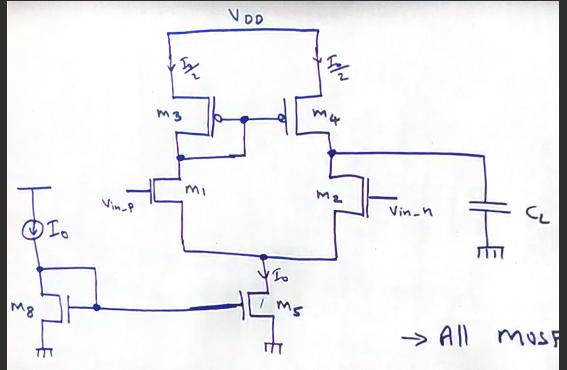

→ All mosf

$+ \quad -$

V_{in}



$r_{o4} \parallel r_{o2}$

$$\therefore \frac{V_o}{r_{o4} \parallel r_{o2}} + \frac{V_o}{\frac{1}{g_m2}} + g_m V_{in} = 0$$


$$\# \frac{V_o}{V_{in}} = \frac{-g_m (r_{o2} \parallel r_{o4})}{1 + g_m C_L (r_{o2} \parallel r_{o4})}$$

Single pole System:

dc gain

$$= g_m (r_{o2} \parallel r_{o4})$$
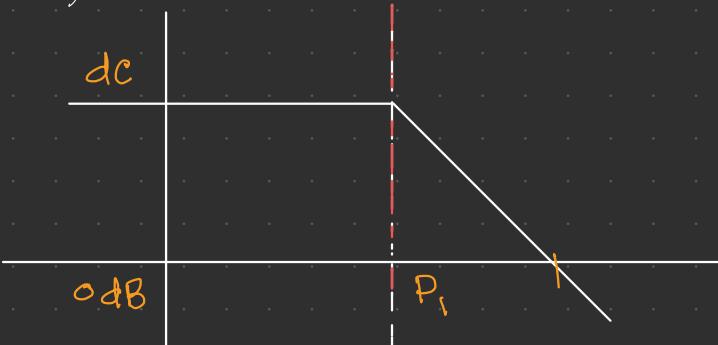
$$P_i = \frac{-1}{(r_{o4} \parallel r_{o2}) C_L}$$



$$\text{Gain Bandwidth} = \frac{g_m}{s C_L} \quad G.BW = \frac{g_m r_{o2}}{2\pi C_L}$$

$$f_{m1,2} = 2\pi \times C_L \times G.BW = 2\pi \times 10\text{pF} \times 5\text{MHz}$$

$$f_{m1,2} = 314.16 \text{Hz}$$

Finding $(\frac{W}{L})$ of m_1, m_2 :

$$I_D = \frac{\mu_n C_{ox} \frac{W}{L}}{2} [V_{GS} - V_T]^2$$

$$\frac{\partial I}{\partial V_{GS}} = g_m = \mu_n C_{ox} \frac{W}{L} [V_{GS} - V_T]$$

$$g_m^m = \frac{\mu_n C_{ox} \frac{W}{L} [V_{GS} - V_T]^2}{2} \times 2$$

$$= 2 I_D \mu_n C_{ox} \frac{W}{L}$$

$$\left(\frac{W}{L}\right) = \frac{g_m^m}{2 I_D \mu_n C_{ox}}$$

$$\therefore \frac{W}{L} \text{ of } m_1 = m_2 \approx 6.57$$



$$\left(\frac{W}{L}\right)_{m_1, m_2} \approx 7$$

① Finding M_S from minimum ICMR (-ve):

give \rightarrow ICMR (-ve) \approx

ICMR minimum = 0.8V

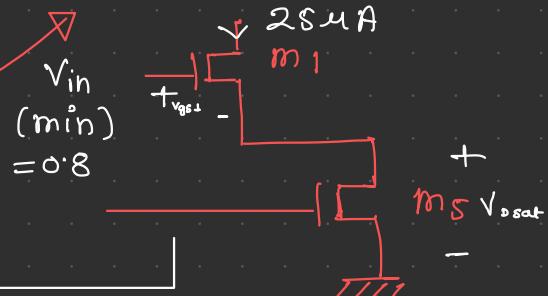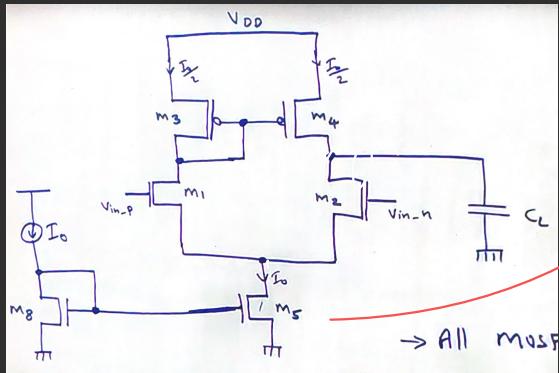UMC 180 nm process
 $V_{DD} = 1.8V$
 $A_v = 100, 40 \text{ dB}$
 $C_L = 10 \text{ pF}$
 $ICMR \approx 1.6V$
 $ICMR = 0.8V$
 $SR = 5V/\mu\text{sec}$
Power < 3 mW
Gain b.w = 5 MHz



$$V_{in} > V_{gs1} + V_{Dsat}$$

$$0.8 > V_{gs1} + V_{Dsat}$$

$$V_{gs} = ?$$

$$I_o = \frac{1}{2} \mu_n C_o \frac{W}{L} [V_{gs} - V_t]^2$$

$$0.8 > 0.6 + V_{Dsat}$$

$$= 2.8 = \frac{300 \mu}{2} (7) [V_{gs} - 0.45]^2$$

$$V_{gs} = 0.6$$

$$\therefore V_{Dsat} \leq 0.2$$

$$I_{D5} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (0.2)^V$$

$$\therefore \left(\frac{W}{L}\right)_5 = 8 \cdot 33 \approx 9 = \left(\frac{W}{L}\right)_8$$



Current Mirror

○ ALL (W/L) (i) $(W/L)_{1,2} = 7$

(ii) $(W/L)_{3,4} = 84$

(iii) $(W/L)_{5,8} = 9$




So, $(W/L)_5 = (W/L)_8$

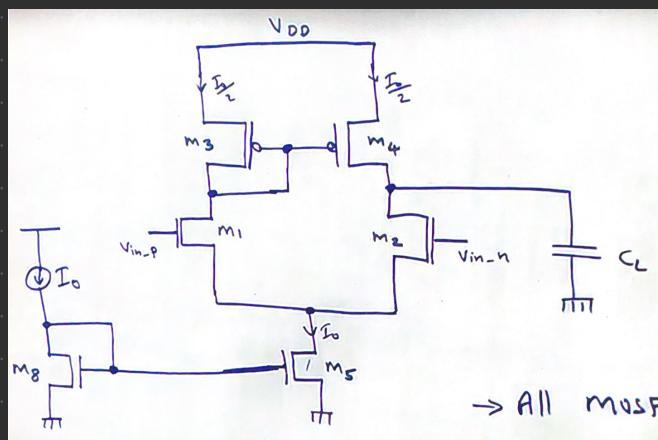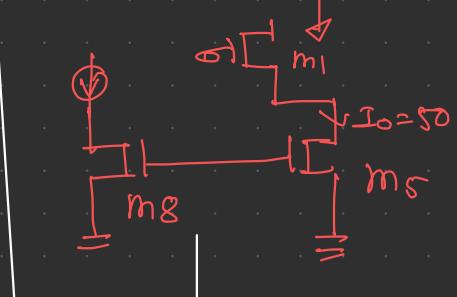

Diff. op-amp could not generate that much gain.




Design of two-stage op-amp

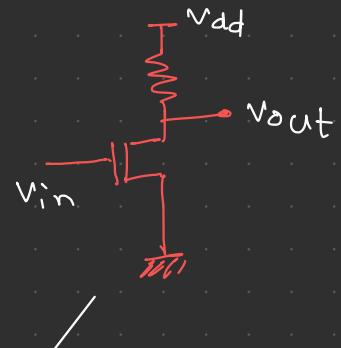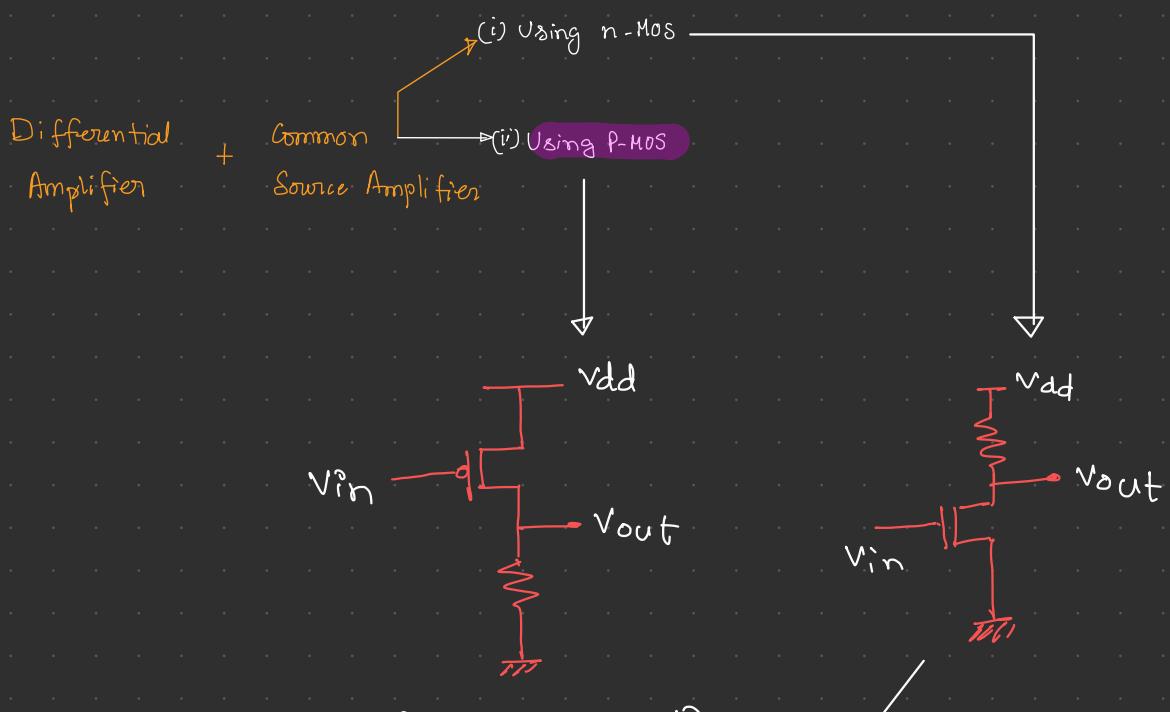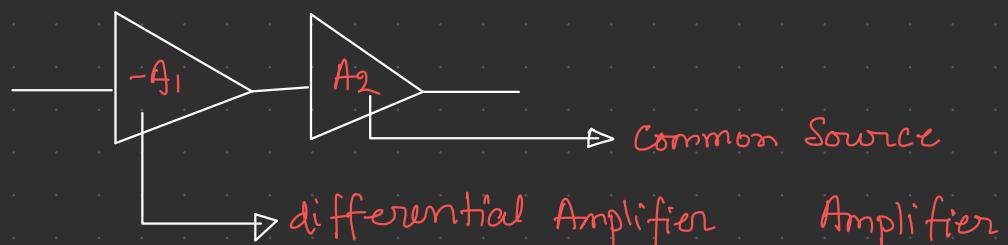


Not Recommended
Swing will be limited


Both Together:


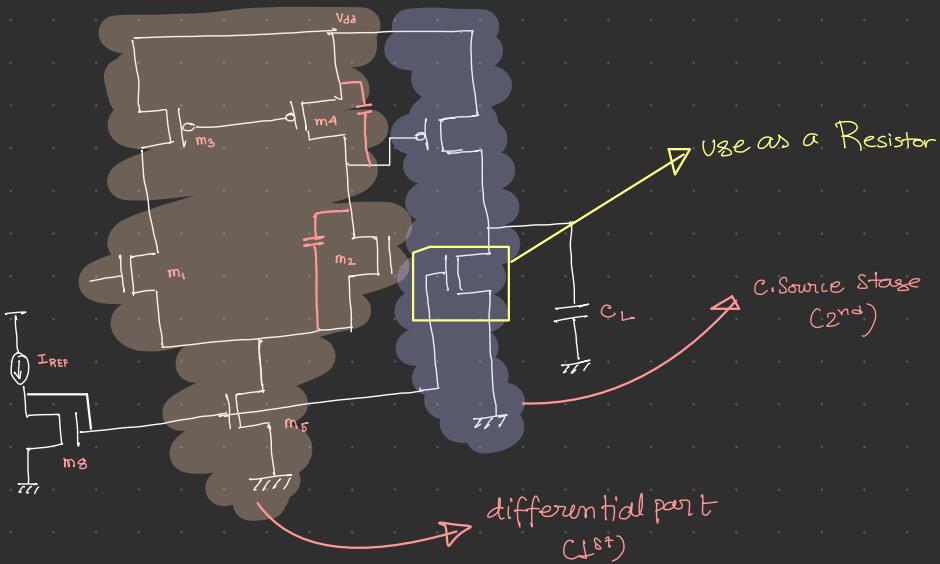


Recall 1st stage:

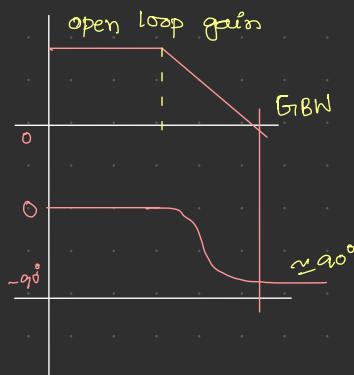

② Two stage port:

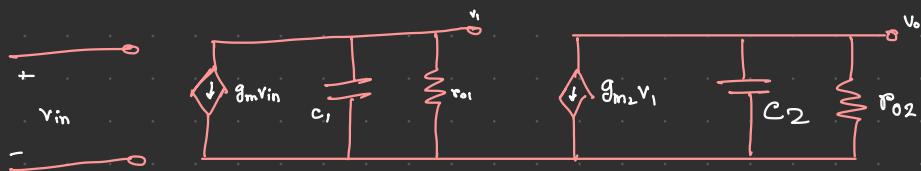

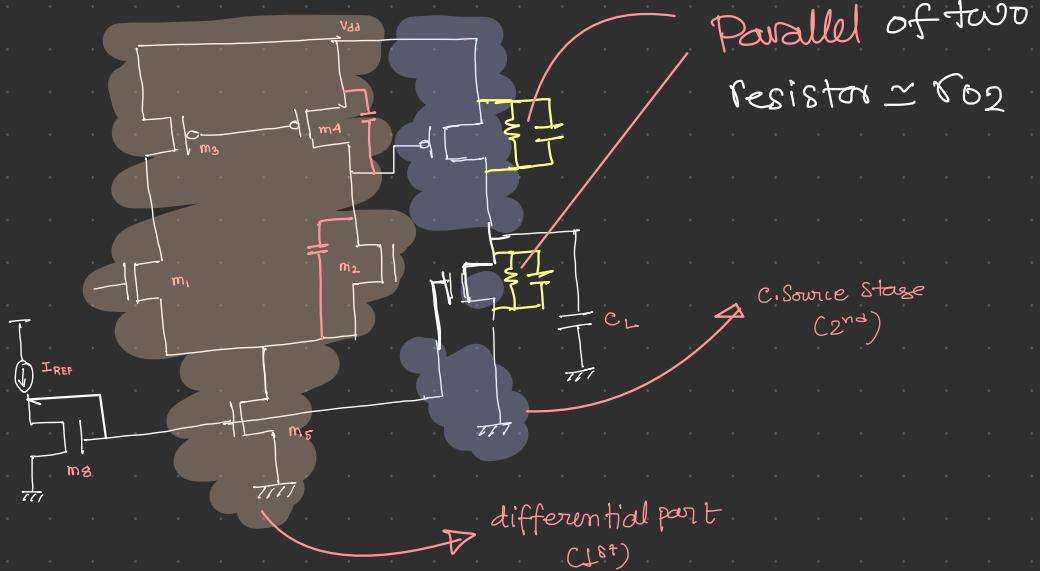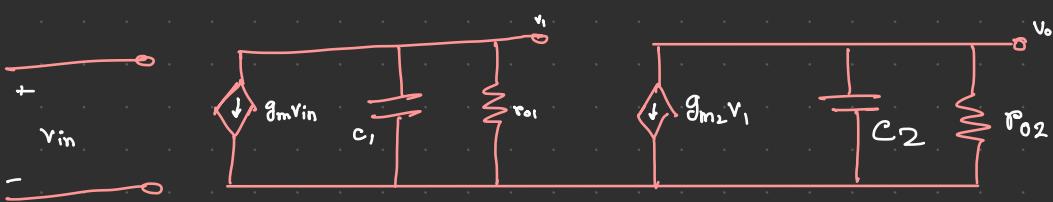

Two pole system:


$$P_1 = \frac{1}{R_{O1} C_1}$$

$$P_2 = \frac{1}{R_{O2} C_2}$$



$$P_1 = \frac{1}{r_{o1} C_1}$$

$$P_2 = \frac{1}{r_{o2} C_2}$$

By using Dominant Pole Concept

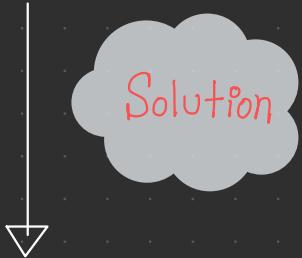

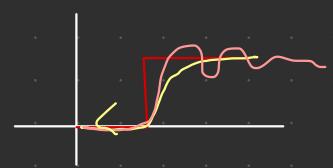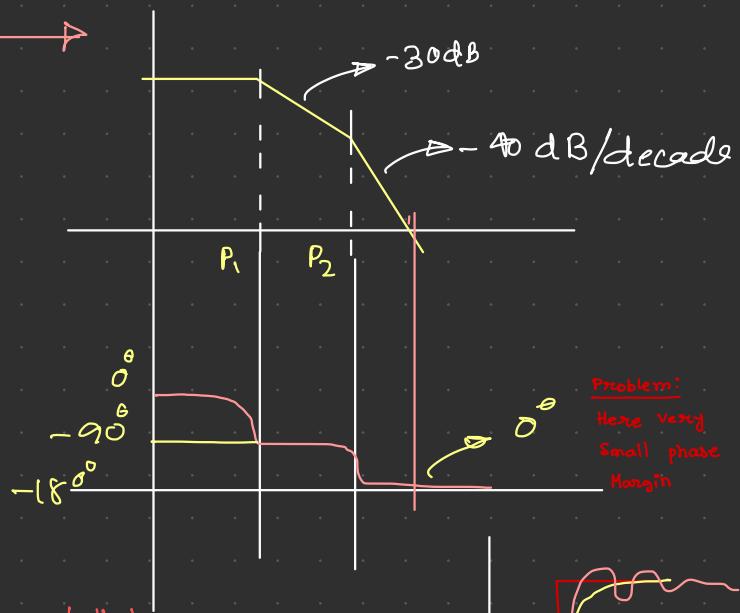Try to shift P_1 pole left side such that
 P_2 comes after crossing 0dB / gain 1.



Compensation

$$P_1 = \frac{1}{r_{o1} C_1}$$

$$P_2 = \frac{1}{r_{o2} C_2}$$


Consists of

load capacitance

minimum phase Margin
 $= 45^\circ$ or 60° (good)

So we don't have that much control
 in C_2

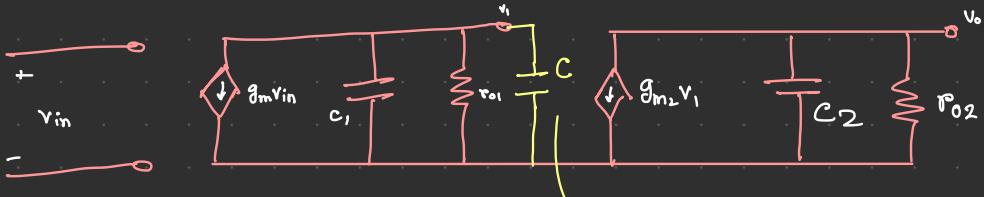We try to increase
 the value of C_1
 So we can shift
 the pole towards left..





$$\text{so, } P_i = \frac{1}{r_{o1}(c_1 + C)}$$

C should be big enough

additional capacitance

parallel with c_1
 $(c + c_1)$

□ Miller Effect

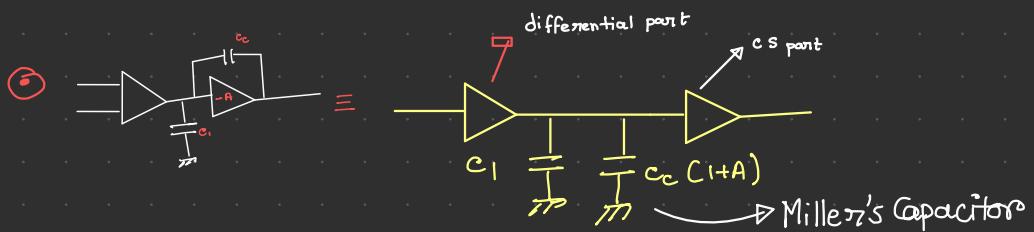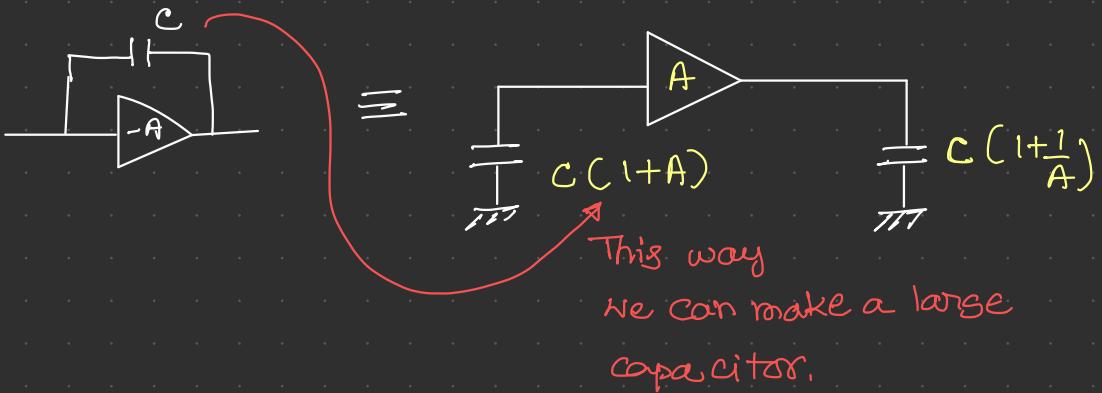


$$P_i = \frac{1}{r_{o1}[(c_1 + C_c(1+A))]}$$

pole left shift


Initial Pole: —

After adding capacitor: —

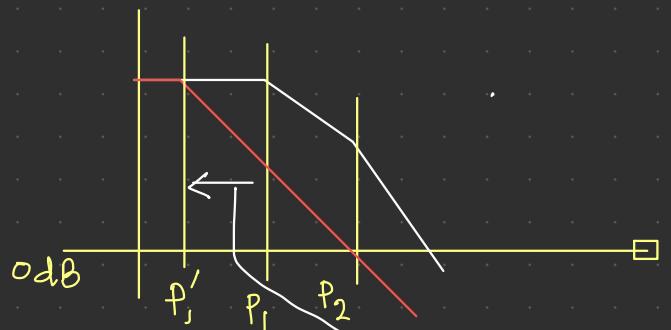
$$P'_1 = \frac{1}{R_{O1} [C_1 + C_C(1+A)]}$$



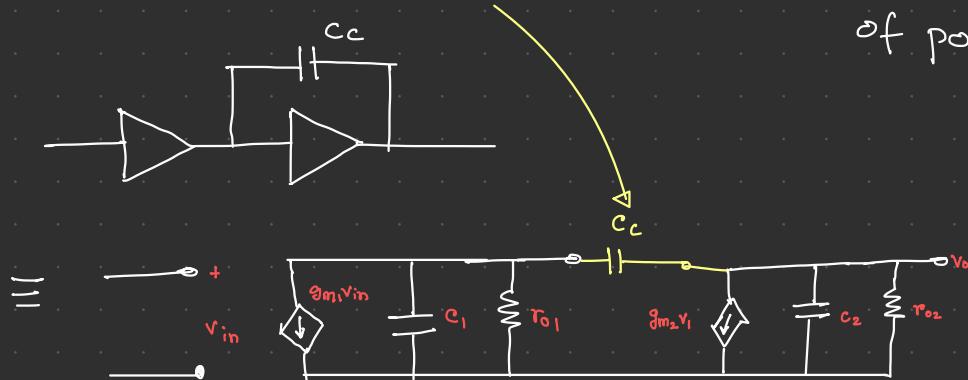$C_C \rightarrow$ Compensated Capacitance



TWO Stage Op-Amp

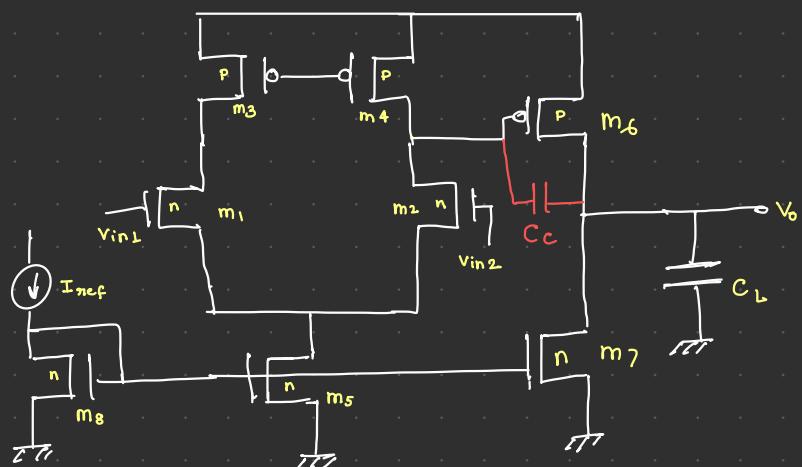


Design of Two Stage OP-Amp

→ Key points: Phase margins → Pole, Zero, G.B.W.

Slew rate


Swing Limits

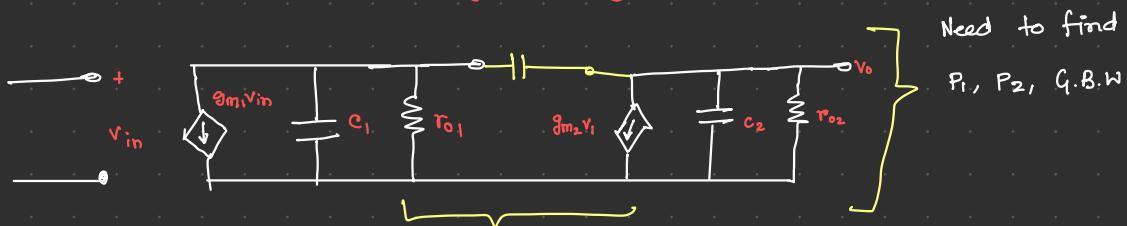


We can not use
Miller's Theorem
to find Transfer
function


Because:

- ① pole splitting
- ② Zeros.

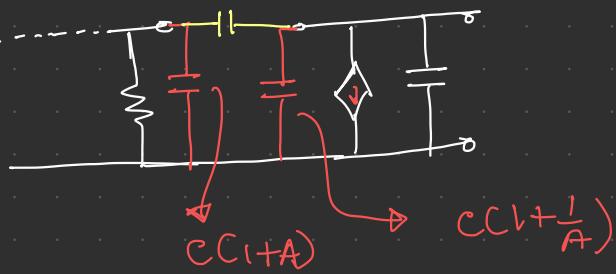

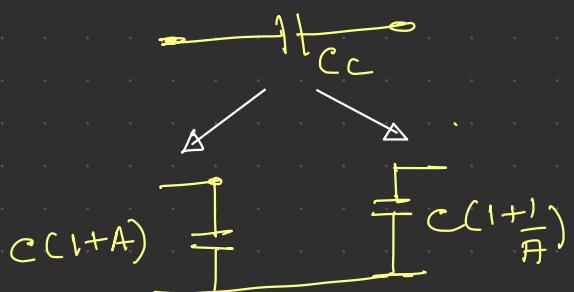in high Frequency C_C got short ckt. But if we apply Miller's Theorem Then that will not happen in high frequency due to the divide in capacitances.



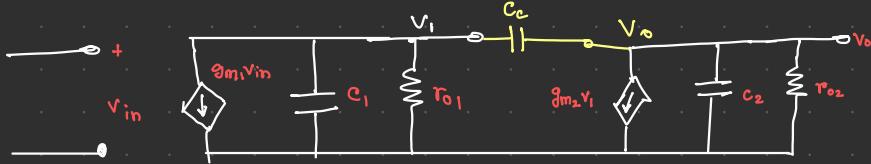

Aim to find $\frac{v_o}{v_{in}} = \frac{v_i}{v_{in}} \times \frac{v_o}{v_i}$

KCL @ node v_i ,

$$\frac{v_i}{R_{o1}} + \frac{v_i}{1/sC_1} + g_{m1}v_{in} + \frac{v_i - v_o}{1/sC_c} = 0$$

$$sC_1v_i + \frac{v_i}{R_{o1}} + g_{m1}v_{in} + (v_i - v_o) sC_c = 0$$

$$v_i = \frac{v_o sC_c R_{o1} - g_{m1} R_{o1} v_{in}}{1 + sR_{o1}(C_1 + C_c)}$$

$$\rightarrow v_o [s(C_2 + C_c) + R_{o2}]$$

$$= \frac{v_o sC_c R_{o1} - g_{m1} R_{o1} v_{in}}{1 + sR_{o1}(C_c + C_2)} [sC_c - g_{m2}]$$

KCL @ v_o ,

$$\frac{v_o - v_i}{1/sC_c} + g_{m2}v_i + \frac{v_o}{1/sC_2} + \frac{v_o}{R_{o2}} = 0$$

$$sC_c(v_o - v_i) + g_{m2}v_i + sC_2v_o + \frac{v_o}{R_{o2}} = 0$$

$$v_o [sC_c + sC_2 + \frac{1}{R_{o2}}] = v_i [sC_c - g_{m2}]$$

Transfer function of Two Stage Op-Amp:

$$\frac{v_o}{v_{in}} = \frac{g_{m1} R_{o1} g_{m2} R_{o2} \left(1 - \frac{sC_c}{g_{m2}} \right)}{s^2 [R_{o1} R_{o2} (C_1 C_2 + C_1 C_c + C_2 C_c) + s [R_{o2} (C_c + C_2) + R_1 (C_c + C_2) + C_c g_{m2} R_{o1} R_{o2}]] + 1}$$

→ (i)

$$\frac{V_o}{V_{in}} = \frac{g_{m1}r_{o1} g_{m2} r_{o2} \left(1 - \frac{s C_c}{g_{m2}} \right)}{s^2 \left[r_{o1} r_{o2} (C_1 C_2 + C_1 C_C + C_2 C_C) + s [r_{o2} (C_C + C_2) + R_1 (C_C + C_1) + C_C g_{m2} r_{o1} r_{o2}] \right] + 1}$$

Standard Transfer function for two pole systems

$$\frac{V_o}{V_{in}} = \frac{A_{DC} \left(1 - \frac{s}{Z} \right)}{\left(1 + \frac{s}{P_1} \right) \left(1 + \frac{s}{P_2} \right)}$$

1 zero
Two pole

We need to find Z , P_1 , P_2 and put in the equation

$$\frac{A_{DC} \left(1 - \frac{s}{Z} \right)}{1 + s \left[\frac{1}{P_1} + \frac{1}{P_2} \right] + s^2 \left[\frac{1}{P_1 P_2} \right]}$$

co-efficient of 's' is $\frac{1}{P_1}$

Considering $P_1 \ll P_2$

$$\frac{1}{P_1} = r_{o2} (C_C + C_2) + r_{o1} (C_C + C_1) + C_C g_{m1} r_{o1} r_{o2}$$

Comparatively gain of one larger than other stage

~~Approx~~

$$P_1 \approx \frac{1}{g_{m2} r_2 r_1 C_C}$$

Co-efficient of s is $\frac{1}{P_1 P_2}$

$$\frac{1}{P_1 P_2} = \frac{1}{R_1 R_2 (C_1 C_2 + C_1 C_C + C_2 C_C)}$$

$$P_2 = \frac{g_m_2 R_2 R_1 C_C}{R_1 R_2 [C_1 C_2 + C_1 C_C + C_2 C_C]} \xrightarrow{\text{Small}} \frac{g_m_2 R_2}{C_1 C_2 + C_1 C_C + C_2 C_C} \xrightarrow{\text{big}}$$

$$P_2 = \frac{g_m_2 C_C}{C_2 C_C} = \frac{g_m_2}{C_2}$$

$$P_1 = \frac{1}{g_m_1 R_1 C_C}$$

$$P_2 = \frac{g_m_2}{C_2}$$

$$Z = \frac{g_m_2}{C_C}$$

DC gain $\rightarrow s=0$ at equation (i)

$$A_{DC} = g_m_1 R_1 g_m_2 R_2$$

Gain Bandwidth Calculation:


$$= DC \text{ gain} \times P_i$$

$$R_1 = r_{o1}, \quad R_2 = r_{o2} \\ = \frac{g_m_1 g_m_2 R_2 \times 1}{g_m_2 R_1 R_2 C_C}$$


$$= \frac{g_m_1}{C_C}$$

Current Mirror

Slew rate:

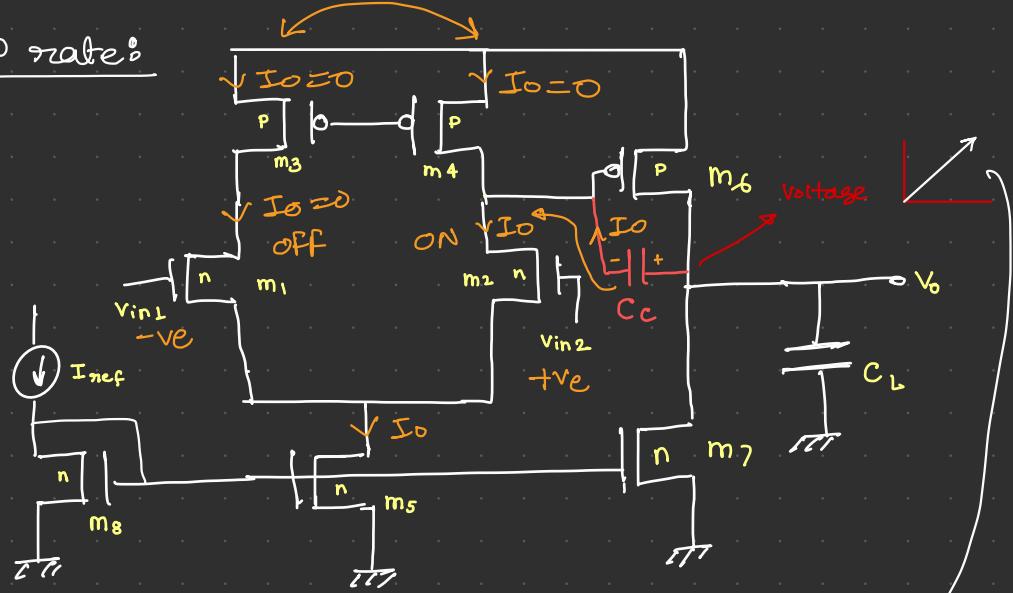

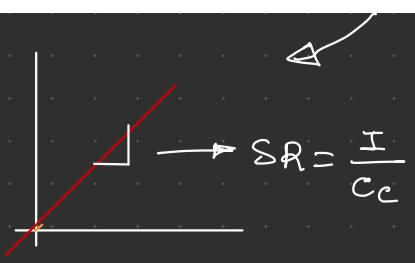
case I:
 m_1 is off so
 m_2 is on
 m_1 has no current so
 m_3 has no current so
 m_4 has no current



→ So, The current flowing through m_5 is flow from m_2 and coming from C_c


The voltage at that point is like a straight line passing through origin and the slope is

the slew rate = $\frac{I}{C_c}$

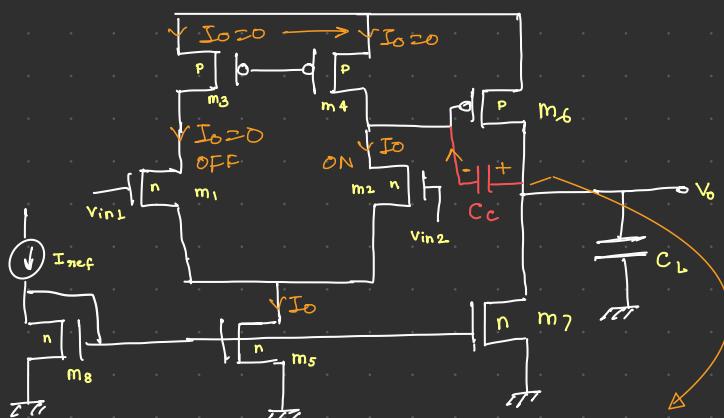

case-I



$\frac{-}{+}$
So, voltage is increasing

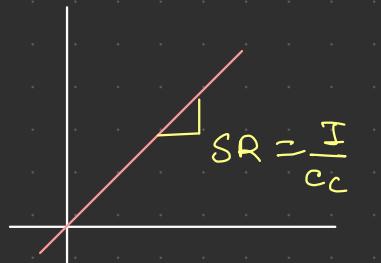

positive


case II: m_1 is ON $\rightarrow m_2$ is off

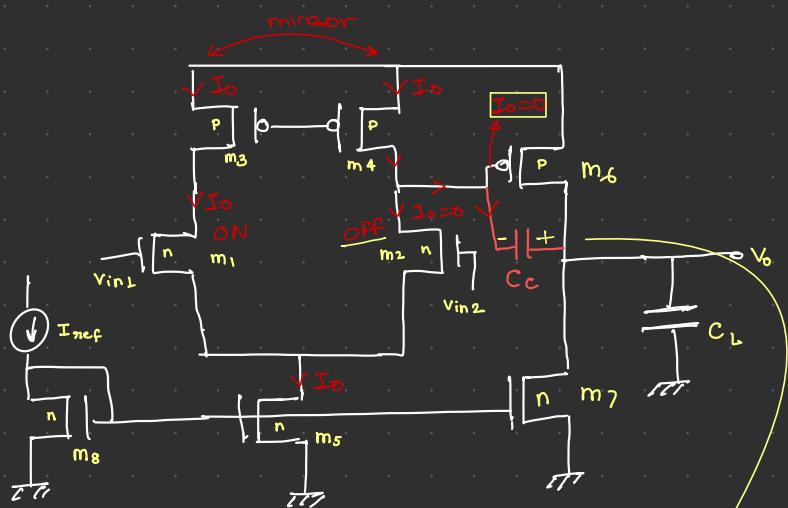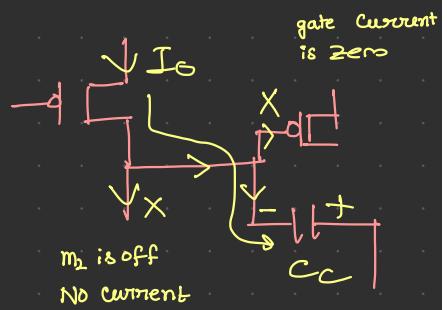I_o is flowing through m_5 , m_1 , m_3 and so m_4 due to mirroring and then it has no way but to flow through the capacitor C_c



Slow scale

$$\propto \frac{I_o}{C_c}$$

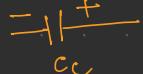

Phase Margin θ


To get a good Phase Margin

P_2 should be far from G.B.W

Point [Try to shift P_2 towards Right]

$$\text{Zero} \geq 10 \text{ GBW}$$
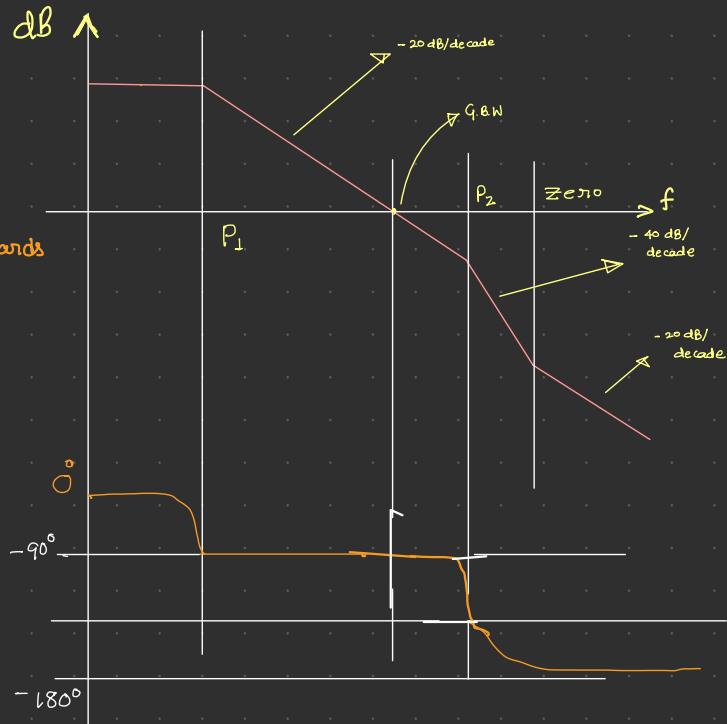
$$\frac{V_o}{V_{in}} = \frac{A_{DC} \left(1 - \frac{S}{Z} \right)}{\left(1 + \frac{S}{P_1} \right) \left(1 + \frac{S}{P_2} \right)}$$




Angle of Transfer function!

$$\angle \frac{V_o}{V_{in}} = -\tan^{-1}\left(\frac{\omega}{Z}\right) - \tan^{-1}\left(\frac{\omega}{P_1}\right) - \tan^{-1}\left(\frac{\omega}{P_2}\right)$$

A phase margin of 60° is preferable and requires at least 45° of phase Margin.

so, we need to find the relation to get that much p.M.
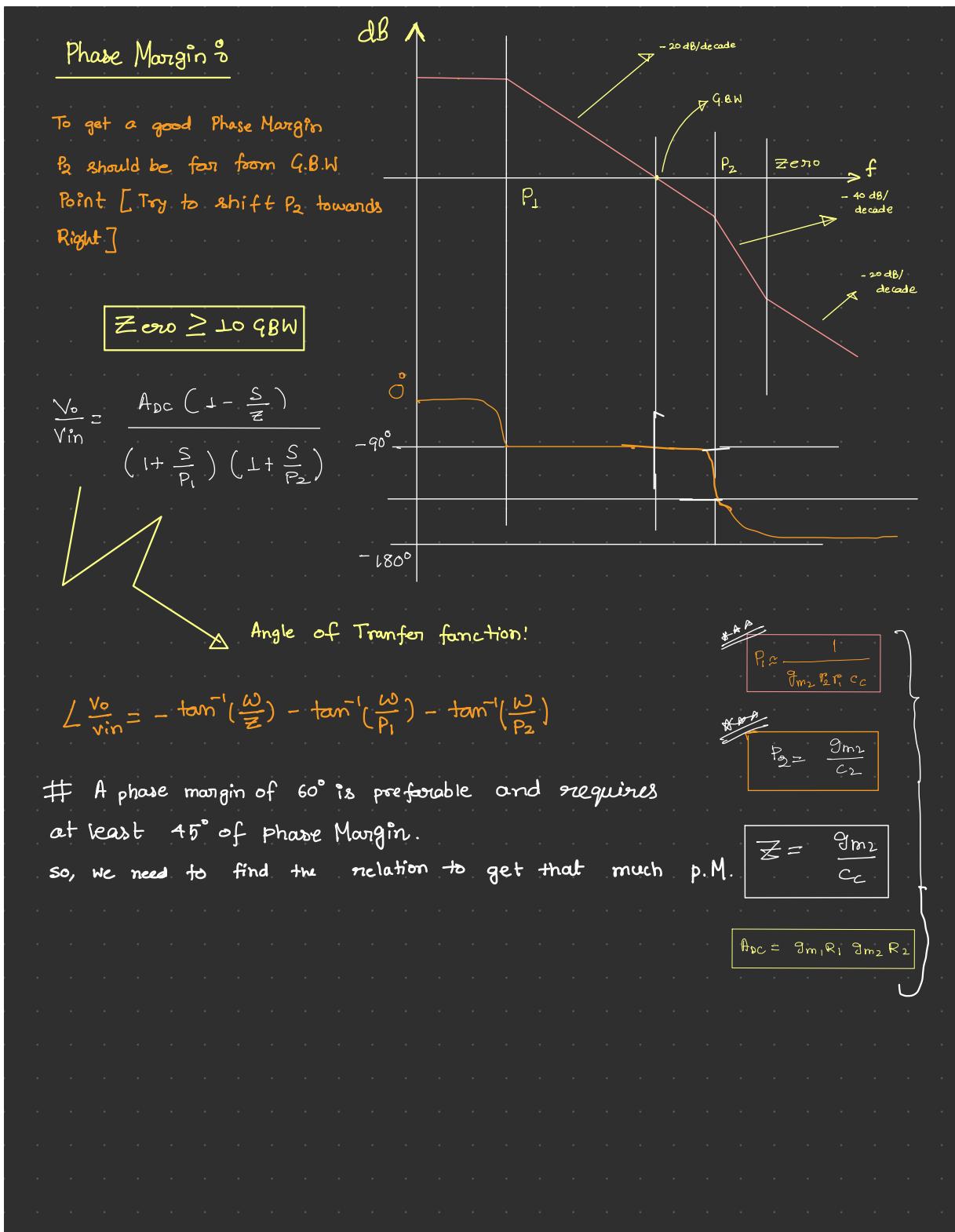
$$\begin{aligned} Z &= \frac{g_m 2}{C_C} \\ g_m 2 &= \frac{g_m 1 R_1 g_m 2 R_2}{C_C} \end{aligned}$$



$$\angle \frac{V_o}{V_{in}} = -\tan^{-1}\left(\frac{\omega}{Z}\right) - \tan^{-1}\left(\frac{\omega}{P_1}\right) - \tan^{-1}\left(\frac{\omega}{P_2}\right)$$

$$P_1 Z = \frac{1}{g_m_2 R_2 C_C}$$

This angle should give at least 60° or 45° of P.M.

We are calculating the P.M.

at

$$f = G.B.W$$

$$\angle \frac{V_o}{V_{in}} \quad | \quad \omega = G.B.W$$

$$= -\tan^{-1}\left(\frac{G.B.W}{Z}\right) - \tan^{-1}\left(\frac{G.B.W}{P_1}\right) - \tan^{-1}\left(\frac{G.B.W}{P_2}\right)$$

$$= -\tan^{-1}\left(\frac{1}{10}\right) - \tan^{-1}\left[\frac{g_m_1}{C_C} \times g_m_2 R_2 R_1 C_C\right] - \tan^{-1}\frac{G.B.W}{P_2}$$

$$= -\tan^{-1}\frac{1}{10} - \tan^{-1}\left[g_m_1 g_m_2 R_2 R_1\right] - \tan^{-1}\frac{G.B.W}{P_2}$$

$$-180^\circ + PM = -5.71 - 90 - \tan^{-1}\frac{G.B.W}{P_2}$$

$$PM = 84.29 - \tan^{-1}\left[\frac{G.B.W}{P_2}\right] \Rightarrow \text{general Formula}$$

Case I

for $PM = 60^\circ$

$$60 = 84.29 - \tan^{-1}\frac{G.B.W}{P_2}$$

$$\tan^{-1}\frac{G.B.W}{P_2} = 24.29$$

$$\frac{G.B.W}{P_2} = 0.4513$$

$$P_2 \geq 2.2 G.B.W$$


Case II

for $PM = 45^\circ$

$$P_2 \geq 1.22 G.B.W$$

$\tan^{-1}(\text{Big Value}) \approx 90^\circ$

DC gain

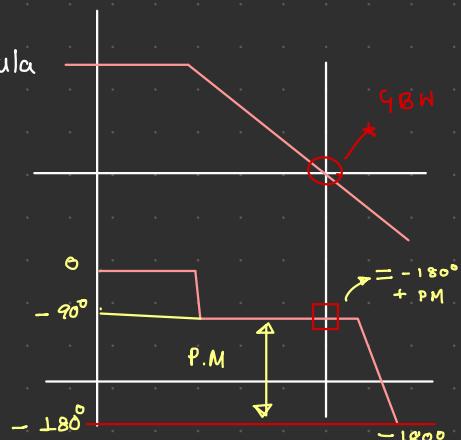

All Parameters Together:

$$P_1 = \frac{1}{g_{m_2} r_1 r_2 C_C}$$

$$P_2 = \frac{g_{m_2}}{C_2}$$

$$A_{dc} = g_{m_1} r_1 g_{m_2} r_2$$

$$Z = \frac{g_{m_2}}{C_C}$$

$$Z = 10 \text{ GBW}$$

$$Q_{BW} = \frac{g_{m_1}}{C_C}$$

$$P_2 \geq 2 \cdot 2 Q_{BW}$$

For 60° Phase Margin

Calculations:

$$Z = \frac{g_{m_2}}{C_C} = 10 \text{ GBW}$$

$$\Rightarrow \frac{g_{m_2}}{C_C} = 10 \frac{g_{m_1}}{C_C}$$


$$\Rightarrow g_{m_2} = 10 g_{m_1}$$

$$P_2 \geq 2 \cdot 2 Q_{BW}$$

$$\frac{g_{m_2}}{C_2} \geq 2 \cdot 2 \frac{g_{m_1}}{C_C}$$

$$\frac{10 g_{m_1}}{C_2} \geq 2 \cdot 2 \frac{g_{m_1}}{C_C}$$

$$C_C \geq 0.22 C_2$$

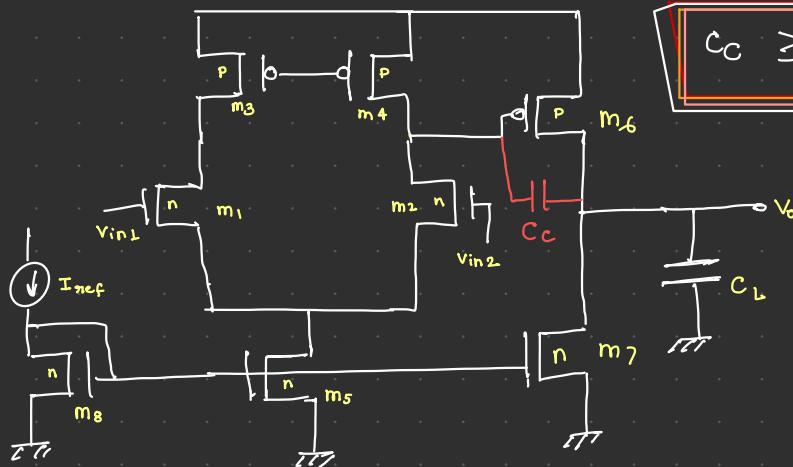

- # C_C should be 0.22 times of C_2 , g_{m_2} should be 10 times g_{m_1} , zero should be 10 times Q_{BW} to make phase margin 60° which is desirable

Assumptions taken: $Z = 10 \text{ GBW}$, $\omega_m^{-1} (\text{large}) = 900$

$$\frac{1}{P_1} + \frac{1}{P_2} \approx \frac{1}{P_1} \quad P_2 \gg P_1 \quad C_2 C_C \gg C_1 C_C, C_1 C_2$$

Here, C_C is the compensation capacitance and $C_2 = C_L$

$C_2 = \text{equal capacitance of 2nd stage}$
which is C_L here,
so, $C_2 = C_L$

① Design Specification: [Process: 180 nm]

DC gain: $1000 = 60 \text{ dB}$

GBW: 30 MHz

P.M: $\geq 60^\circ$

Power: 300 μW

Slew rate: 20 V/msec

ICMR (+): 1.6V

ICMR (-): 0.8V

$C_L = 2 \text{ pF}$

Vdd: 1.8V

$$\rightarrow L_{min} = 180 \text{ nm} \quad L \geq 2L_{min}$$

$$L = 360 \text{ nm}$$

① All MOSFET should be in "Saturation"

Region"

② I_o \longrightarrow Slew Rate

③ M_3, M_4 \longrightarrow ICMR + (max)

④ M_1, M_2 \longrightarrow Gain \times B.W

⑤ M_8 \longrightarrow I_o & M_5

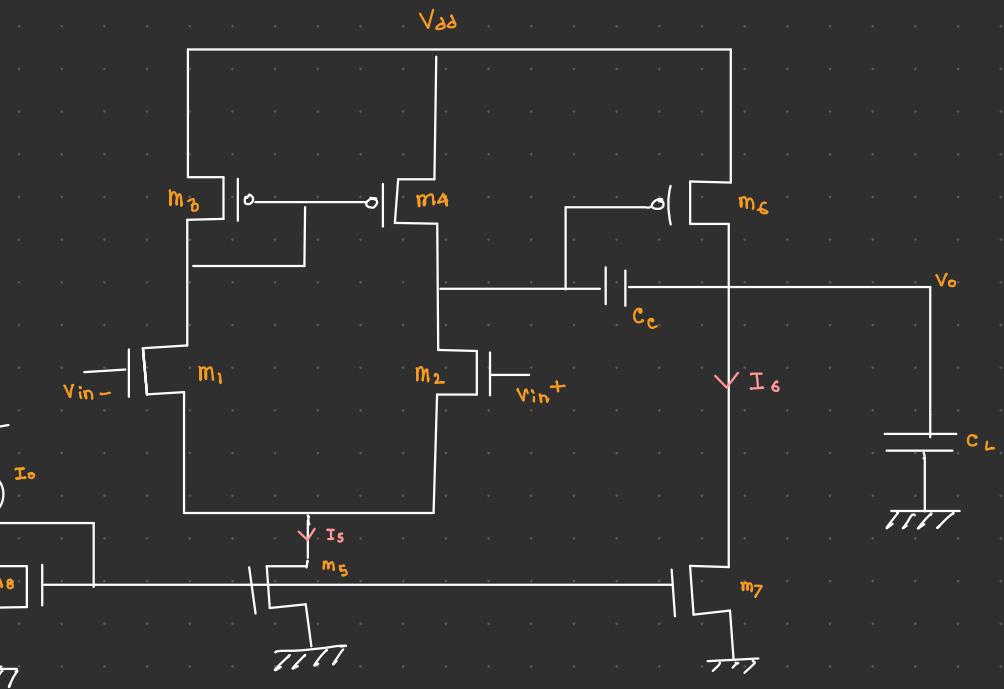


Fig: Two Stage Op-Amp

$ICMR(+)$

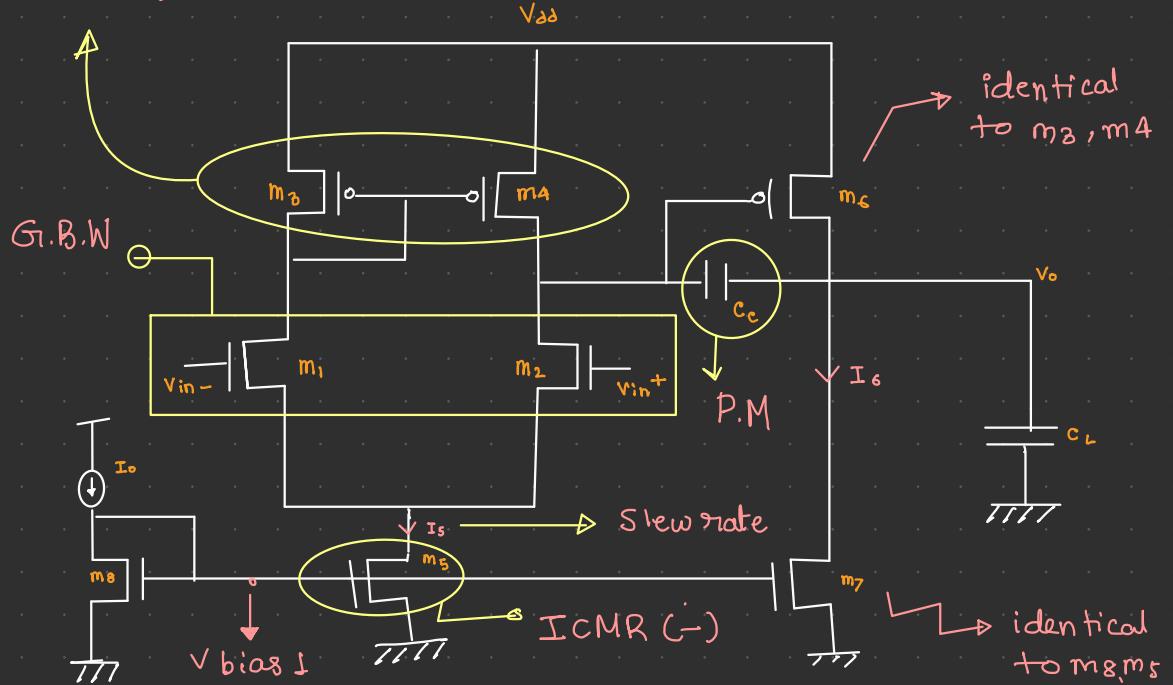


Fig: Two Stage Op-Amp

Given: ① Channel length $L = 500 \text{ nm}$

② To get PM of $60^\circ \rightarrow C_C \geq 0.22 C_L$

$$C_C \geq 0.22 \times 2 \text{ pF}$$

Condition for 60° phase margin

For simulation purpose we choose $C \geq 440 \text{ fF}$

$C = 800 \text{ fF}$ ← Assume

③ Slew rate = $\frac{I_S}{C_C}$

$$I_S = \text{slew rate} \times C_C$$

$$= \frac{20 \text{ V}}{\mu \text{ s}} \times 800 \text{ fF}$$

$$I_S = 16 \text{ mA} \rightarrow I_S = 20 \text{ mA}$$

Assume

④ m_1, m_2 From G.B.W

$$\text{We know, } g_{m1} = G_{BW} \times C_C \times 2\pi$$

$$= 30 \text{ MHz} \times 800 \text{ fF} \times 2\pi$$

$$g_{m1} = 150.79 \mu \text{A} \approx 160 \mu \text{A}$$

We know,


$$\left(\frac{W}{L}\right) = \frac{g_m^v}{\mu_{nCox} \times 2 I_D}$$

For, m_1, m_2

$$\frac{I_S}{2} = I_D(m_1, m_2)$$

$$2 I_D = I_S$$
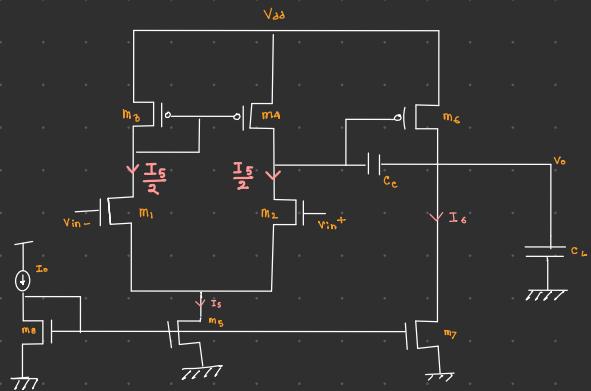
$$\frac{W}{L} = \frac{g_m^v}{\mu_{nCox} \times I_S}$$



$$\mu_{nCox} = 300 \mu$$

$$\frac{W}{L} = \frac{160^v}{300 \times 20} \approx 4.266$$

$$\left[\frac{W}{L}\right]_{m_1, m_2} = 5$$

Design of m_3, m_4 : m_3, m_4 are identical

- ④ m_3 is in saturation for all time because it is diode connected.
 - ⑤ So if V_{in} goes high m_1 will go in Triode Region.
 - ⑥ So, m_1 to be in saturation

$$V_{DS} > V_{GS} - V_t$$

$$v_p > v_q - v_{t_1}$$

$$V_g < V_D + V_{t1} \quad | \quad \equiv V_{in} < V_{D1} + V_{t1}$$

$$\therefore V_{in(max)} = V_{D1} + V_{t1}$$

$$\text{From (11)} \quad V_d = V_{dd} - \left[\sqrt{\frac{2 I_3}{\beta}} + |V_{t3}| \right] \quad (14)$$

$$V_d = V_{ad} - V_{sg3} \quad \text{--- (11)}$$


$$I_3 = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)$$

$$I_3 = \frac{\beta}{2} [v_{GS} - v_t]^2$$

$$V_{GS} = \sqrt{\frac{2I_3}{\rho}} + \left(V_t \right)_s \quad (iii)$$

$$\rightarrow \text{From (1)} \quad V_{in} \leq V_{D1} + V_{t1}$$

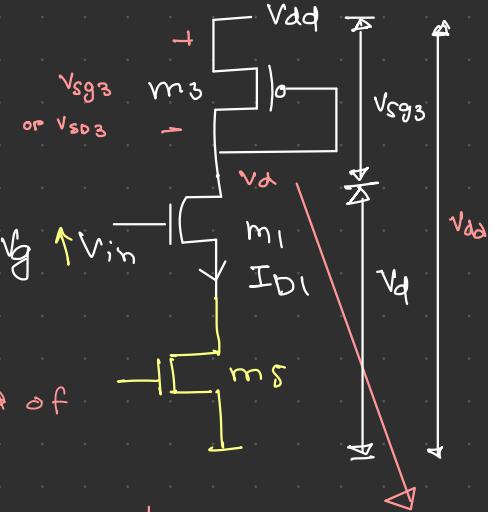To make Min
 max less than
equal to RHS,
RHS should be
minimum.



$$V_{in(max)} \leq [V_{D1} + V_{t1}]_{min}$$

$$V_{in\ (max)} \leq (V_{DI} + V_{TI})_{min}$$

$$\text{or, } \text{ICMR}(\pm) \leq \text{Vad} - \left[\sqrt{\frac{2I_{03}}{\beta}} + |\text{V}_{t3}| \right] + \text{V}_{tc} \text{ (min)}$$

$$ICMR(t) \leq V_{dd} - \sqrt{\frac{2ID^3}{\beta}} - [V_{t2}]_{\max} + V_{t1(\min)}$$

Because
if Vt_3 in max then
only the whole quantity
goes minimum

$$ICMRC(t) \leq V_{dd} - \sqrt{\frac{2I_{d3}}{\beta_3}} - |V_{t3}| + |V_{t1}|$$

We know, $M_n \text{Co} = 300M$

$$M_p \text{ Cox} = 60.4$$

$$\beta_3 = \mu_p \cos\left(\frac{w}{L}\right) -$$


putting the value of β_3 and find $(\frac{w}{L})$

$$I_{CMR}(+) \leq v_{ad} = \sqrt{\frac{2 I_{23}}{\mu_{in} C_{\infty} \left(\frac{W}{L}\right)_3}} - |V_{t3}|_{max} + |V_t|_{min}$$

$$\text{or} \quad \sqrt{\frac{2 I_{D3}}{M_{\text{Cox}} \left(\frac{W}{L}\right)_3}} \leq V_{dd} - ICNR(\%) - |V_{t3}|_{\max} + |V_{t1}|_{\min}$$

$$\alpha_1 \frac{2 ID_3}{\mu_p C_{ox} \left(\frac{W}{L}\right)_3} \leq \left[V_{dd} - ICMR(t) - |V_{t3}|_{max} + |V_{t1}|_{min} \right]^+$$

$$\left[\frac{W}{L} \right]_3 \geq \frac{1}{M_p \text{Cox} \left[V_{dd} - \Sigma CMR(\pm) - \frac{|V_{t3}|_{max}}{|V_{t1}|_{min}} \rightarrow |V_{t1}|_{min} \right]^{\gamma}}$$

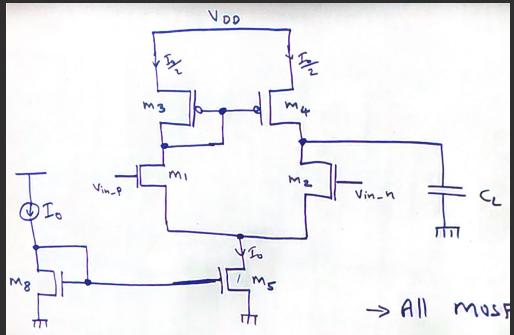

We are taking

$$V_{t3} \text{ (max)} \approx 502 \text{ mv} \rightarrow 510 \text{ mv (max)}$$

Apply $V_{CM} = 0.8$ and
 1.6 v to get

V_{t_3} max, min

U_{ti} max, min in

differential pair.

\therefore from $\left[\frac{w}{L} \right]$

$$\left[\frac{W}{L} \right]_{m_3, m_4}$$

$$= \frac{V_{P\text{Cox}}}{V_{ad} - [ICMR(t) - V_{t_3(\max)} - V_{t_1(\min)}]}$$

$$= \frac{2 \times 10^4}{69 \times [5.8 - 5.6 - 0.51 + 0.47]^2}$$

= 13.02

$$V_{dd} = 1.2$$

$$I_{D3} = \frac{I_{DS}}{2} = 10.4 A$$

$$M_p \cos x = 60M$$

$$M_{\text{lock}} = 300 M_\odot$$


$$ICMR(\theta) = 1.6_r$$

$$Vt_3(\max) = 0.51$$


$$V_{t_1}(\text{min}) = 0.47$$

$$\left[\frac{W}{L} \right]_{m_3, m_4} \approx 14$$

design of Ms:

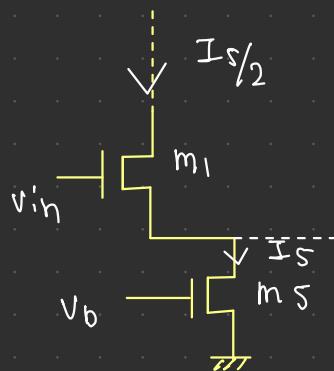

From ICMR (-)

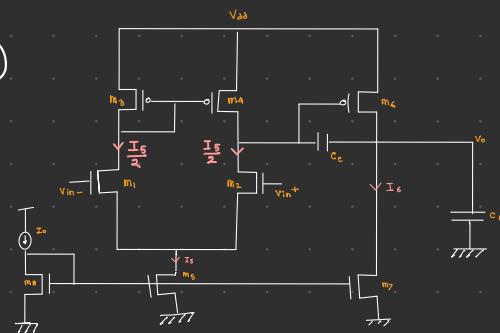

$$v_g = v_{in} |_{m_1} \quad v_s |_{m_1} = V_d |_{m_5}$$

By decrease in v_{in} we decrease V_d → To support the current v_{gs} almost remain constant.

Condition for m_5 to be in saturation while decreasing $v_{in} \downarrow$.

$$\rightarrow v_{in} \downarrow \quad V_d \downarrow$$

for m_1

$$\text{for } m_5 \quad \downarrow V_{ds} > v_g - V_{t5}$$

m_5 will go to triode Region.

∴ How should we decrease v_{in} so, m_5 will be in Saturation.


at $V_d = V_{dsat}$ = min value of V_d to keep m_5 in saturation.

So, $v_{in} \geq v_{gs} + V_{dsat}$ (min) at V_{dsat} is min v_{in} goes min by keeping m_5 in saturation

$$ICMR(-) \geq \left[\frac{2 I_{D1}}{\beta_1} + V_{t1}(\max) + V_{dsat} \right]$$

We need the voltage across $m_5 = V_{dsat}(s)$
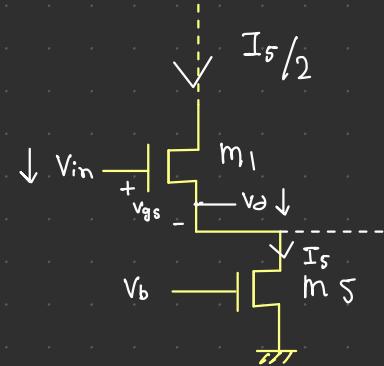
$$V_{dsat}(s) \geq ICMR(-) - \sqrt{\frac{2 I_{D1}}{\beta_1}} - V_{t1}(\max)$$



$$V_{in}(\min) \geq V_{gs1} + V_{dsat}$$

$$= ICMR(-) \geq V_{gs1} + V_{dsat}$$

$$= ICMR(-) \geq \left[\sqrt{\frac{2 I_{D1}}{\beta_1}} + V_{t1} \right]_{\max} + V_{dsat}$$

Putting all values:

$$V_{dsat}(S) \geq 0.8 - \sqrt{\frac{2 \times 104}{300 \mu \times 5}}$$

$\therefore V_{dsat}(S) \geq 0.8 - 0.1154 = 0.59$


$V_{dsat}(S) \geq 94.6 \text{ mV}$

0.590V

$V_{t1}(\max)$

From Cadence
differential
pair

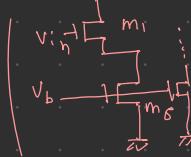Note! We got $V_{dsat} = 94.6 \text{ mV}$ for which we need to make a large MOSFET $\left(\frac{W}{L} \propto \frac{1}{v_d} \right)$ also the next MOSFET will be large.



$\left[\frac{W}{L} \right]_{m_1} \rightarrow$ if we increase it V_{dsat} will increase

→ Generally we prefer V_a of m_5 is $> 100 \text{ mV}$. So, to make it greater than 100 mV we only can increase $\left[\frac{W}{L} \right]$ of m_1 because other parameters cannot be changed.

So, at $\left[\frac{W}{L} \right]_{m_1} = 5 \rightarrow V_{dsat} \geq 94.6 \text{ mV}$

$\left[\frac{W}{L} \right]_{m_1} = 6 \rightarrow V_{dsat} \geq 108 \text{ mV}$

We know, $I_S = \frac{\mu_n C_{ox}}{2} \left[\frac{W}{L} \right]_S [V_{dsat(S)}]^2$

$$\therefore \left[\frac{W}{L} \right]_S = \frac{2 I_S}{\mu_n C_{ox}} \frac{1}{[V_{dsat(S)}]^2} \approx 12.09$$


$\left[\frac{W}{L} \right]_S = 12 \quad \left[\frac{W}{L} \right]_{L2} = 6$

Design of m_6 : For 60° PM $\rightarrow g_{m6} \geq 10g_{m1}$

$$\therefore g_{m6} \geq 10 g_{m1}$$

$$g_{m6} \geq 10 \times 160 \mu$$

$$g_{m6} \geq 1600 \mu$$

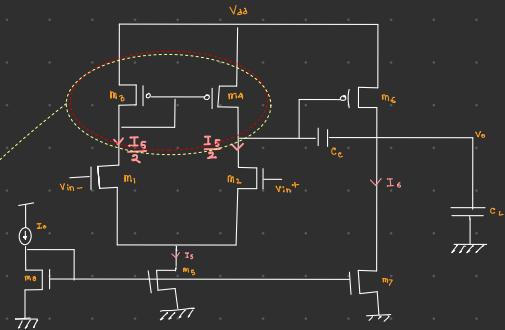

and $V_{GS}|_{m_3} = V_{DS}|_{m_3}$ $\Rightarrow V_{GS}|_{m_4} = V_{GS}|_{m_3} = V_{GS}|_{m_6}$

$\therefore V_{DS}|_{m_3} = V_{DS}|_{m_4} = V_{DS}|_{m_6}$ in case of proper mirroring

So, currents will be proportional

to the W/L of the MOSFET.

$$I_D = \mu_P C_{ox} \frac{W}{L} \left[\frac{V_{GS} - V_t}{2} \right]^2$$

$$\frac{\left(\frac{W}{L}\right)_6}{\left(\frac{W}{L}\right)_4} = \frac{I_6}{I_4}$$

$$\frac{\left(\frac{W}{L}\right)_6}{\left(\frac{W}{L}\right)_4} = \frac{g_{m6}}{g_{m4}}$$

$$g_m = \sqrt{\mu C_{ox} \left(\frac{W}{L}\right) 2 I_D}$$

$$g_{m4} = \sqrt{60 \times 14 \times 2 \times 10} = 129.6 \mu$$

$$\left(\frac{w}{L}\right)_6 = \frac{9m_6}{9m_4} \left(\frac{w}{L}\right)_4 = \frac{1600}{129.61} = 14$$

$$\boxed{\left(\frac{w}{L}\right)_6 = 172.82 \approx 173}$$

Design of m_7 (m_5)

$$\frac{\left(\frac{w}{L}\right)_5}{\left(\frac{w}{L}\right)_7} = \frac{I_5}{I_7}$$

$$\left(\frac{w}{L}\right)_7 = \frac{I_7 \left(\frac{w}{L}\right)_5}{I_5}$$

$$= \frac{125 \mu A \times 12}{20} = 75$$

$$I_6 = \frac{\left(\frac{w}{L}\right)_6}{\left(\frac{w}{L}\right)_4} I_4$$

$$= \frac{174}{14} \times 10$$

$$= 124.28$$

$$\approx 125 \mu A = I_7$$

$$\boxed{\left[\frac{w}{L}\right]_7 = 75 \quad \left[\frac{w}{L}\right]_6 = 173}$$

$$I_S = 204$$

$$C_C = 800 \text{ fF}$$

$$m_{1,2} = 6 = \frac{3}{5} \left[\frac{w}{L}\right]$$


$$m_{3,4} = 14 = \frac{7}{5}$$

$$m_5 = 12 = \frac{6}{5}$$

$$m_6 = 174 = \frac{87}{5}$$


$$m_7 = 75 = \frac{37.5}{5}$$

$$I_6, I_7 = 125 \mu A$$

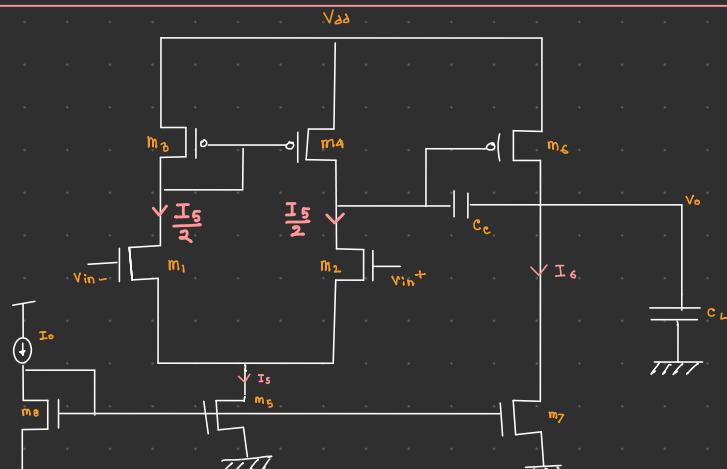

$$\boxed{L = 180 \text{ nm}}$$

Fig: Two Stage Op-Amp

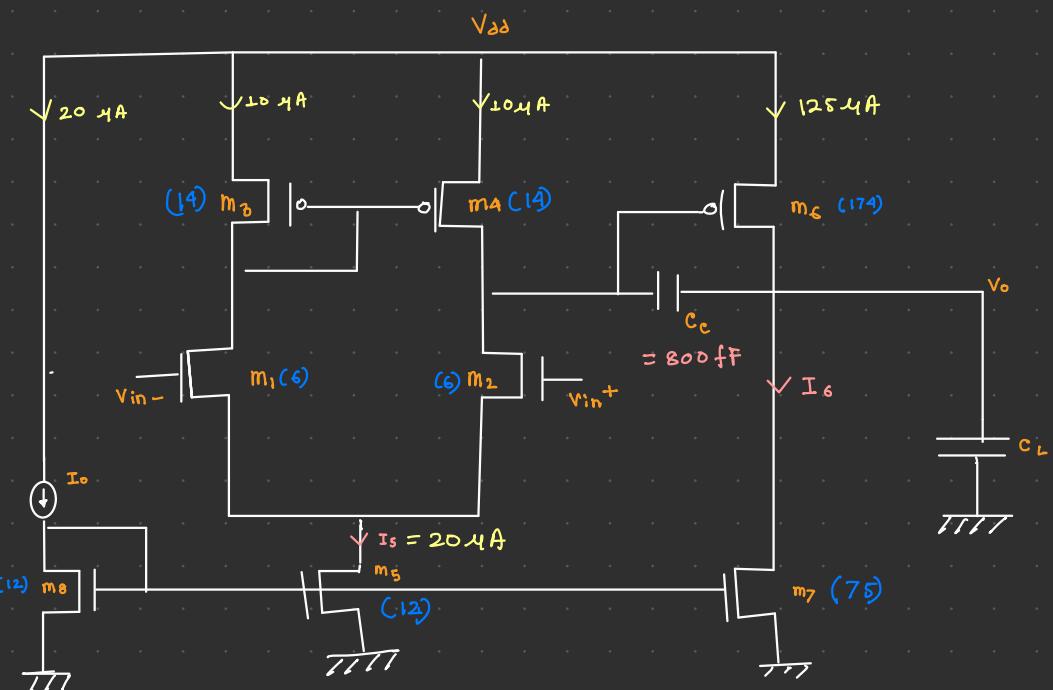

$$\therefore \text{power} = 300 \text{ mW} \quad V_{dd} = 1.8 \quad \therefore I = 166.66 \mu\text{A}$$

$$= 125 + 20 + 10 + 10$$

$$\approx 165 \approx 166.66 \mu\text{A}$$

② Design Specification: [Process: 180 nm]

DC gain: $1000 = 60 \text{ dB}$

GBW: 30 MHz

P.M: $\geq 60^\circ$

Power: $300 \mu\text{W}$

slew rate: $20 \text{ V}/\mu\text{sec}$

ICNR (+): 1.6 V

ICNR (-): 0.8 V

$C_L = 2 \text{ pF}$

$V_{dd} = 1.8 \text{ V}$

Blue no. core

$\left[\frac{W}{L} \right] \text{ ratio}$

$$\rightarrow L_{min} = 180 \text{ nm} \quad L \geq 2L_{min}$$

$$L = 500 \text{ nm}$$

$$\text{Power} = (125 + 20) = 145 \mu\text{A} \times 1.8$$

$$= 261 \text{ mV} < 300 \text{ mW}$$

Practical Design Parameter and Specification

[Cadence]

